

Formation of Z-Bus Matrix

Matlab Code:-

% Universal Z-Bus Building Algorithm (Step-by-Step Output)

clear; clc;

% Network data from the provided circuit image

% Format: [From_Bus, To_Bus, Impedance]

linedata = [

0, 1, 1i*0.25; % Step 1: Adds Bus 1

1, 2, 1i*0.10; % Step 2: Adds Bus 2

1, 3, 1i*0.10; % Step 3: Adds Bus 3

2, 3, 1i*0.10; % Step 4: Link between Bus 2 and Bus 3

0, 2, 1i*0.25 % Step 5: Link from Bus 2 to Reference

];

% Initialize empty Zbus

Zbus = [];

nl = size(linedata, 1);

disp('=== STARTING Z-BUS ALGORITHM ===');

disp(' ');

for i = 1:nl

fb = linedata(i, 1);

tb = linedata(i, 2);

z = linedata(i, 3);

sz = size(Zbus, 1);

```
% TYPE 1: New bus to reference bus
```

```
if (fb == 0 && tb > sz) || (tb == 0 && fb > sz)
```

```
    fprintf('--- STEP %d: Adding Type 1 (New Bus to Ref) ---\n', i);
```

```
    fprintf('Element: Node %d to Node %d, Z = %g + %gi\n', fb, tb, real(z), imag(z));
```

```
    if isempty(Zbus)
```

```
        Zbus = z;
```

```
    else
```

```
        Zbus = [Zbus, zeros(sz, 1); zeros(1, sz), z];
```

```
    end
```

```
% TYPE 2: New bus to an existing bus
```

```
elseif (fb > 0 && fb <= sz && tb > sz) || (tb > 0 && tb <= sz && fb > sz)
```

```
    fprintf('--- STEP %d: Adding Type 2 (New Bus to Existing) ---\n', i);
```

```
    fprintf('Element: Node %d to Node %d, Z = %g + %gi\n', fb, tb, real(z), imag(z));
```

```
    if fb <= sz
```

```
        eb = fb;
```

```
    else
```

```
        eb = tb;
```

```
    end
```

```
    new_col = Zbus(:, eb);
```

```
    new_row = Zbus(eb, :);
```

```
    new_diag = Zbus(eb, eb) + z;
```

```
    Zbus = [Zbus, new_col; new_row, new_diag];
```

```
% TYPE 3: Existing bus to reference bus
```

```
elseif (fb == 0 && tb <= sz) || (tb == 0 && fb <= sz)
```

```
    fprintf('--- STEP %d: Adding Type 3 (Existing to Ref - Kron Reduction) ---\n', i);
```

```
    fprintf('Element: Node %d to Node %d, Z = %g + %gi\n', fb, tb, real(z), imag(z));
```

```
    eb = max(fb, tb);
```

```

new_col = Zbus(:, eb);
new_row = Zbus(eb, :);
new_diag = Zbus(eb, eb) + z;

Z_temp = [Zbus, new_col; new_row, new_diag];
Zbus = Z_temp(1:sz, 1:sz) - (Z_temp(1:sz, sz+1) * Z_temp(sz+1, 1:sz)) / Z_temp(sz+1,
sz+1);

% TYPE 4: Existing bus to existing bus
elseif (fb > 0 && tb > 0 && fb <= sz && tb <= sz)
    fprintf('--- STEP %d: Adding Type 4 (Existing to Existing - Kron Reduction) ---\n', i);
    fprintf('Element: Node %d to Node %d, Z = %g + %gi\n', fb, tb, real(z), imag(z));

    new_col = Zbus(:, fb) - Zbus(:, tb);
    new_row = Zbus(fb, :) - Zbus(tb, :);
    new_diag = Zbus(fb, fb) + Zbus(tb, tb) - 2 * Zbus(fb, tb) + z;

    Z_temp = [Zbus, new_col; new_row, new_diag];
    Zbus = Z_temp(1:sz, 1:sz) - (Z_temp(1:sz, sz+1) * Z_temp(sz+1, 1:sz)) / Z_temp(sz+1,
sz+1);
end

% THIS IS THE ADDED COMMAND TO MAKE STEPS VISIBLE
disp('Resulting Z-Bus Matrix:');
disp(Zbus);
disp(' ');
end

disp('=== FINAL Z-BUS MATRIX REACHED ===');

```

```

PSA_EXP_2_Code.m
1 % Universal Z-Bus Building Algorithm (Step-by-Step Output)
2 clear; clc;
3
4 % Network data from the provided circuit image
5 % Format: [From_Bus, To_Bus, Impedance]
6 linedata = [
7     0, 1, 1i*0.25; % Step 1: Adds Bus 1
8     1, 2, 1i*0.10; % Step 2: Adds Bus 2
9     1, 3, 1i*0.10; % Step 3: Adds Bus 3
10    2, 3, 1i*0.10; % Step 4: Link between Bus 2 and Bus 3
11    0, 2, 1i*0.25 % Step 5: Link from Bus 2 to Reference
12 ];
13
14 % Initialize empty Zbus
15 Zbus = [];
16 nl = size(linedata, 1);
17
18 disp('=== STARTING Z-BUS ALGORITHM ===');
19 disp(' ');
20
21 for i = 1:nl

```

Command Window

```

--- STEP 5: Adding Type 3 (Existing to Ref - Kron Reduction) ---
Element: Node 0 to Node 2, Z = 0 + 0.25i
Resulting Z-Bus Matrix:
    0.0000 + 0.1397i    0.0000 + 0.1103i    0.0000 + 0.1250i
    0.0000 + 0.1103i    0.0000 + 0.1397i    0.0000 + 0.1250i
    0.0000 + 0.1250i    0.0000 + 0.1250i    0.0000 + 0.1750i

=== FINAL Z-BUS MATRIX REACHED ===

```

Result:-

=== STARTING Z-BUS ALGORITHM ===

--- STEP 1: Adding Type 1 (New Bus to Ref) ---

Element: Node 0 to Node 1, $Z = 0 + 0.25i$

Resulting Z-Bus Matrix:

$0.0000 + 0.2500i$

--- STEP 2: Adding Type 2 (New Bus to Existing) ---

Element: Node 1 to Node 2, $Z = 0 + 0.1i$

Resulting Z-Bus Matrix:

$0.0000 + 0.2500i$ $0.0000 + 0.2500i$

$0.0000 + 0.2500i$ $0.0000 + 0.3500i$

--- STEP 3: Adding Type 2 (New Bus to Existing) ---

Element: Node 1 to Node 3, $Z = 0 + 0.1i$

Resulting Z-Bus Matrix:

$0.0000 + 0.2500i$	$0.0000 + 0.2500i$	$0.0000 + 0.2500i$
$0.0000 + 0.2500i$	$0.0000 + 0.3500i$	$0.0000 + 0.2500i$
$0.0000 + 0.2500i$	$0.0000 + 0.2500i$	$0.0000 + 0.3500i$

--- STEP 4: Adding Type 4 (Existing to Existing - Kron Reduction) ---

Element: Node 2 to Node 3, $Z = 0 + 0.1i$

Resulting Z-Bus Matrix:

$0.0000 + 0.2500i$	$0.0000 + 0.2500i$	$0.0000 + 0.2500i$
$0.0000 + 0.2500i$	$0.0000 + 0.3167i$	$0.0000 + 0.2833i$
$0.0000 + 0.2500i$	$0.0000 + 0.2833i$	$0.0000 + 0.3167i$

--- STEP 5: Adding Type 3 (Existing to Ref - Kron Reduction) ---

Element: Node 0 to Node 2, $Z = 0 + 0.25i$

Resulting Z-Bus Matrix:

$0.0000 + 0.1397i$	$0.0000 + 0.1103i$	$0.0000 + 0.1250i$
$0.0000 + 0.1103i$	$0.0000 + 0.1397i$	$0.0000 + 0.1250i$
$0.0000 + 0.1250i$	$0.0000 + 0.1250i$	$0.0000 + 0.1750i$

=== FINAL Z-BUS MATRIX REACHED ===